

Worksheet:

**Drafting circuit diagrams** 


Class:

AU1

## Electrical circuit diagram
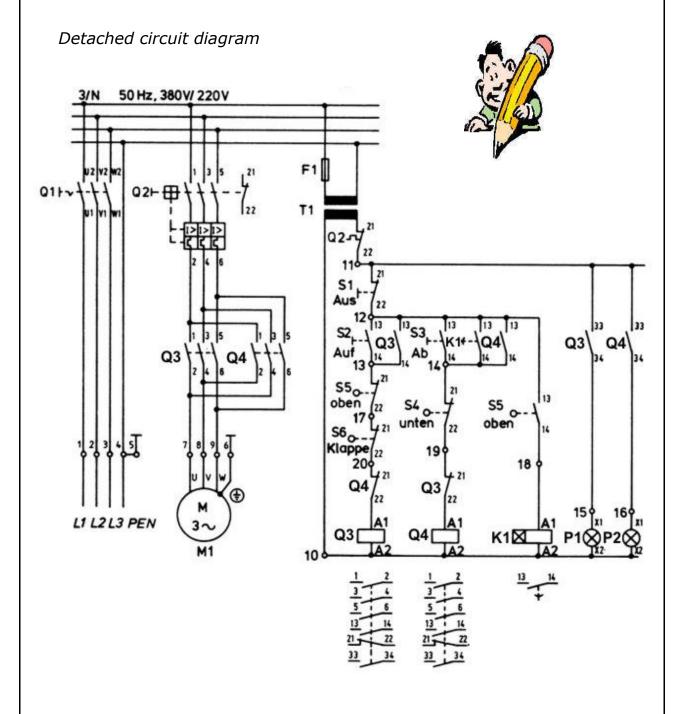
## Task

The detached and the assembled circuit diagrams of a motor control are given. Compare the circuit diagrams. Imagine that contactor Q3 is energized and highlight the current path of contactor Q3 in both auxiliary circuit diagrams.



Datum: 26.01.14 / Roman Moser

Datei: AUF3.2.4\_DraftingCircuitDiagrams\_Ex1




Worksheet:

**Drafting circuit diagrams** 

Class:

AU1

## Assembled circuit diagram

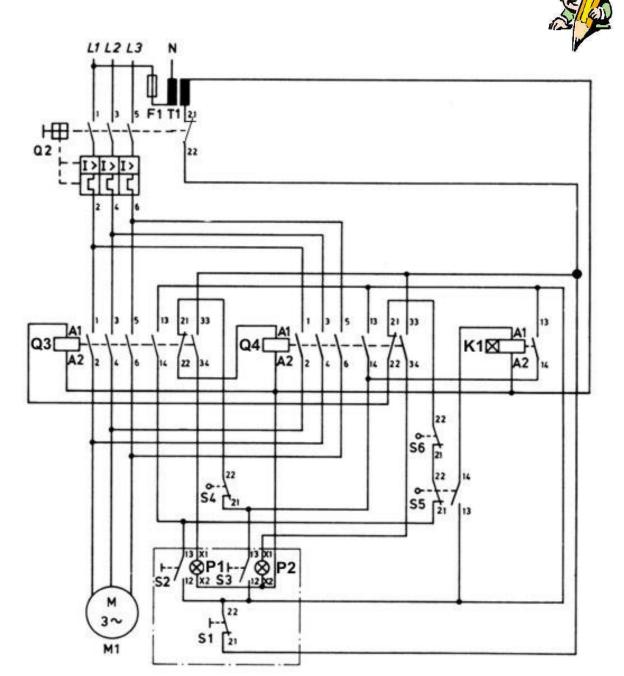

Datum: 26.01.14 / Roman Moser
Datei: AUF3.2.4\_DraftingCircuitDiagrams\_Ex1